

Digital Electronics

CA #1

Name: Mohammad

Last Name: Taghizadeh Givari

Student No: 810198373

Contents


1. Question 1.....	2
Part a.....	2
Part b.....	4
Part g.....	13
2. Question 2.....	16
Part a.....	16
Part b.....	19
Part g.....	25

Question 1:


Transfer characteristic of an inverter

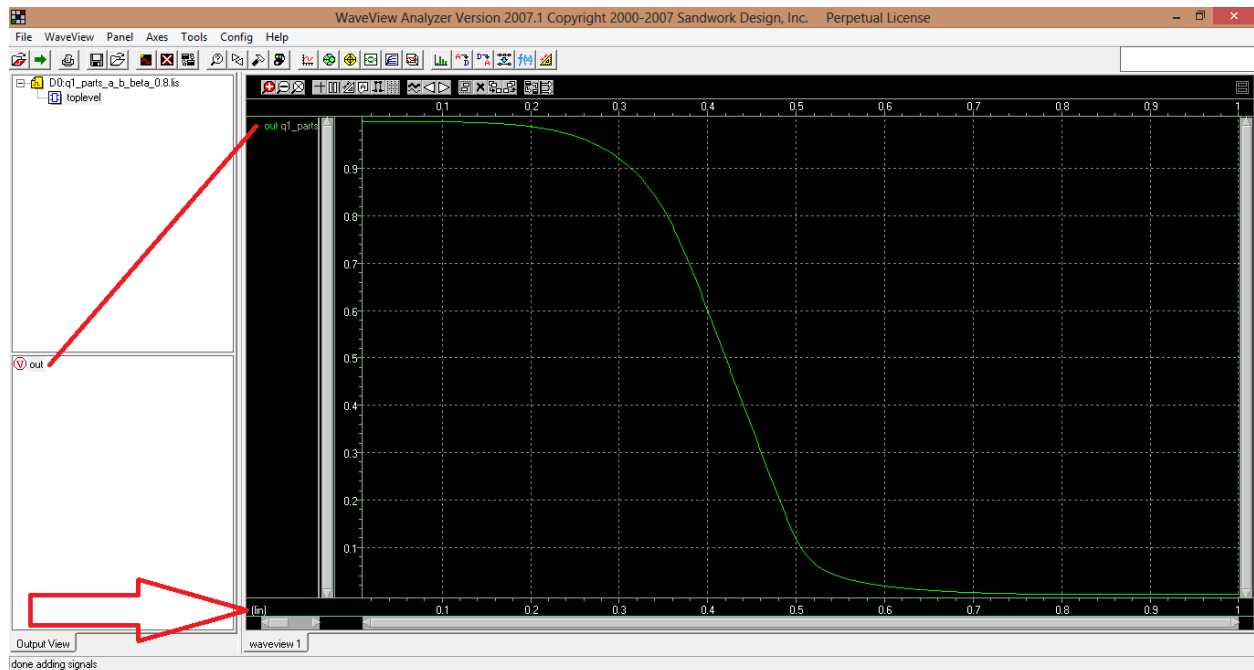Part a:


VTC(Voltage Transfer Characteristic) for $\beta = 0.8$



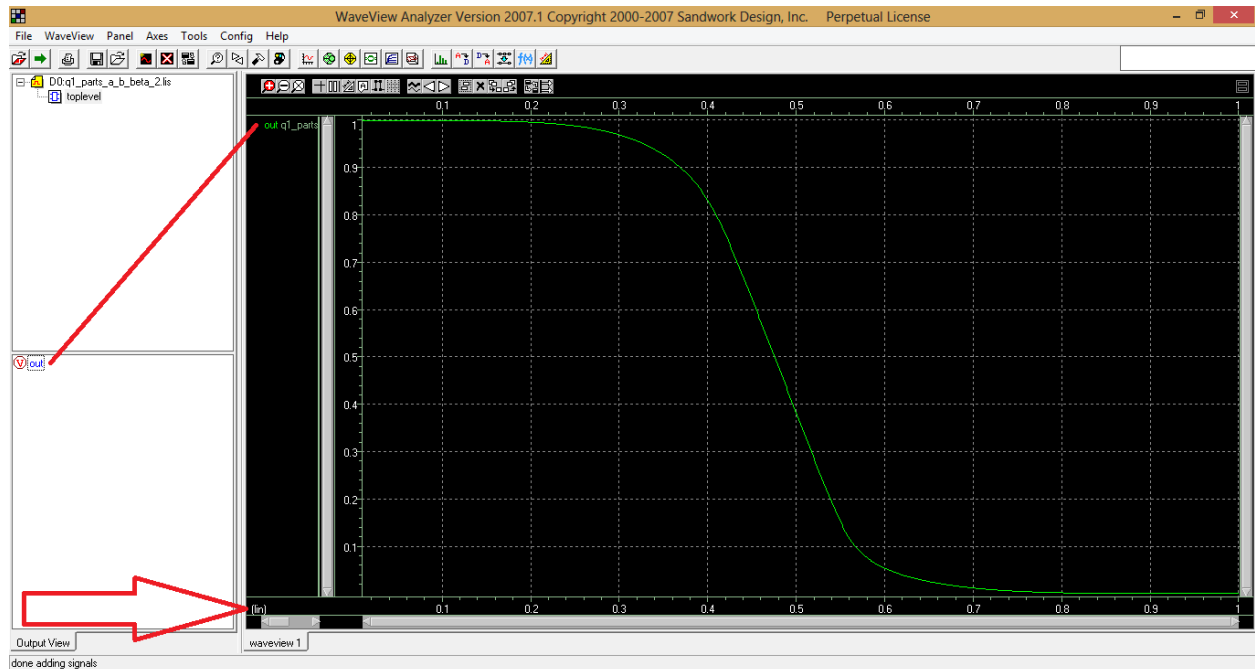VTC(Voltage Transfer Characteristic) for $\beta = 2$




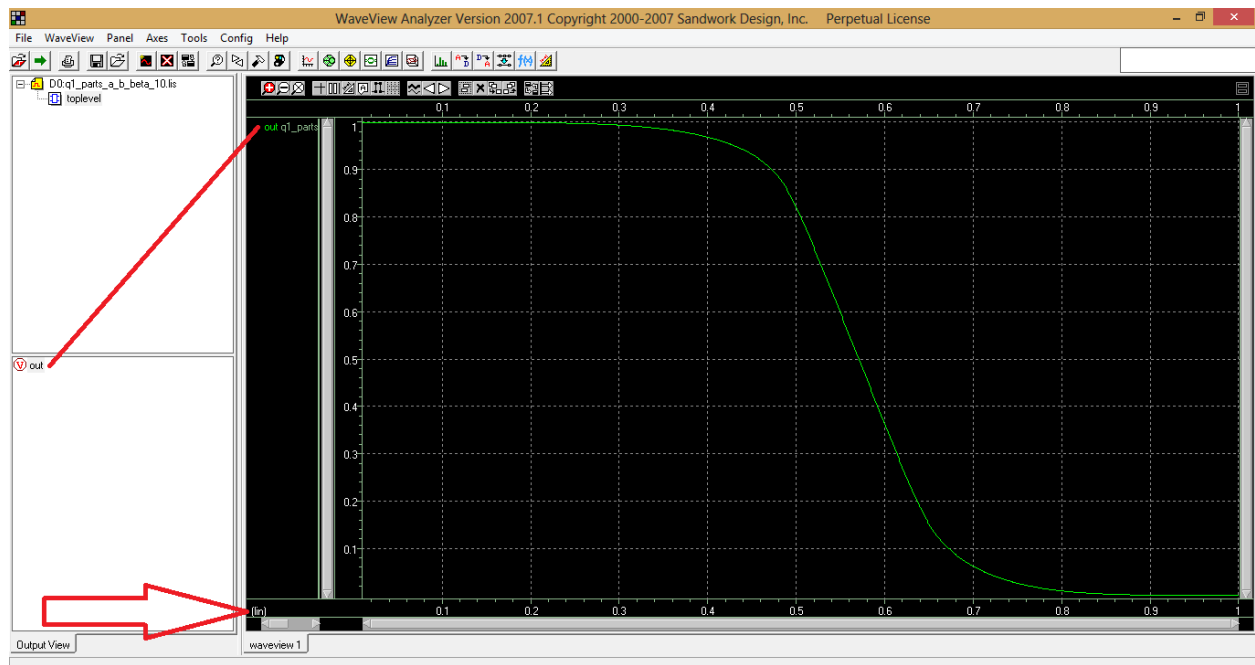VTC(Voltage Transfer Characteristic) for $\beta = 10$



Part b:

$V_{OH}V_{IL}$ for $\beta = 0.8$

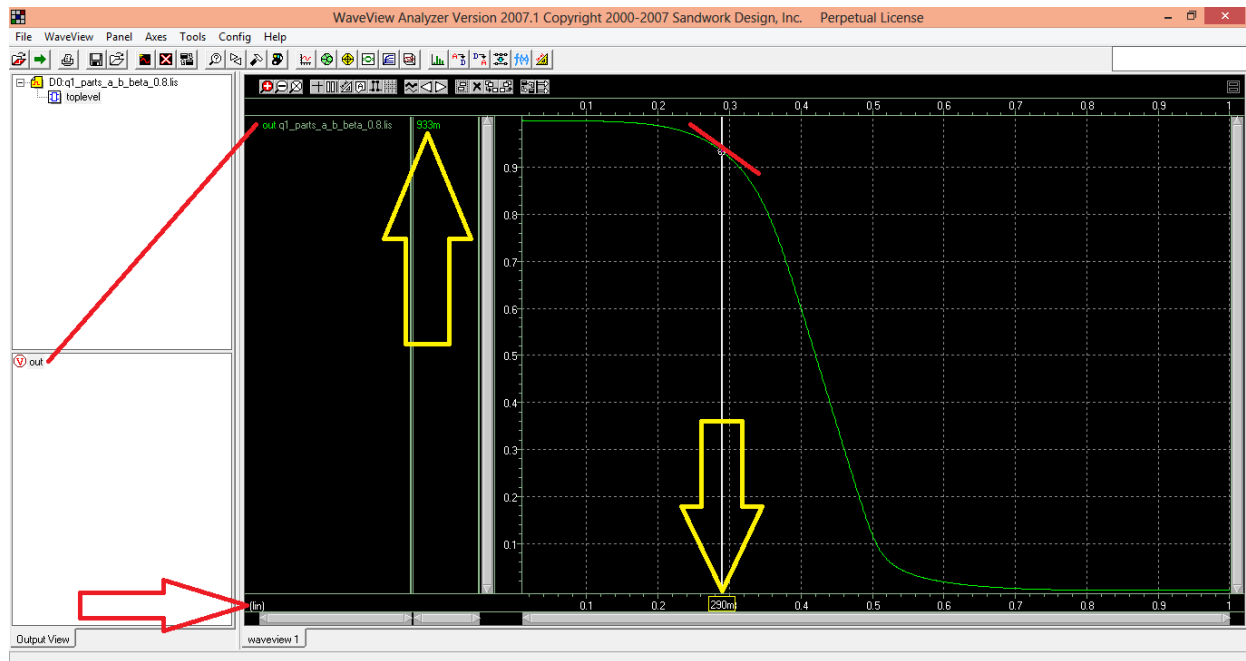


$\Rightarrow V_{OH} = 933 \text{ mV}, \quad V_{IL} = 290 \text{ mV}$

$V_{OL}V_{IH}$ for $\beta = 0.8$




$\Rightarrow V_{OL} = 59.1 \text{ mV}, \quad V_{IH} = 526 \text{ mV}$

V_M for $\beta = 0.8$

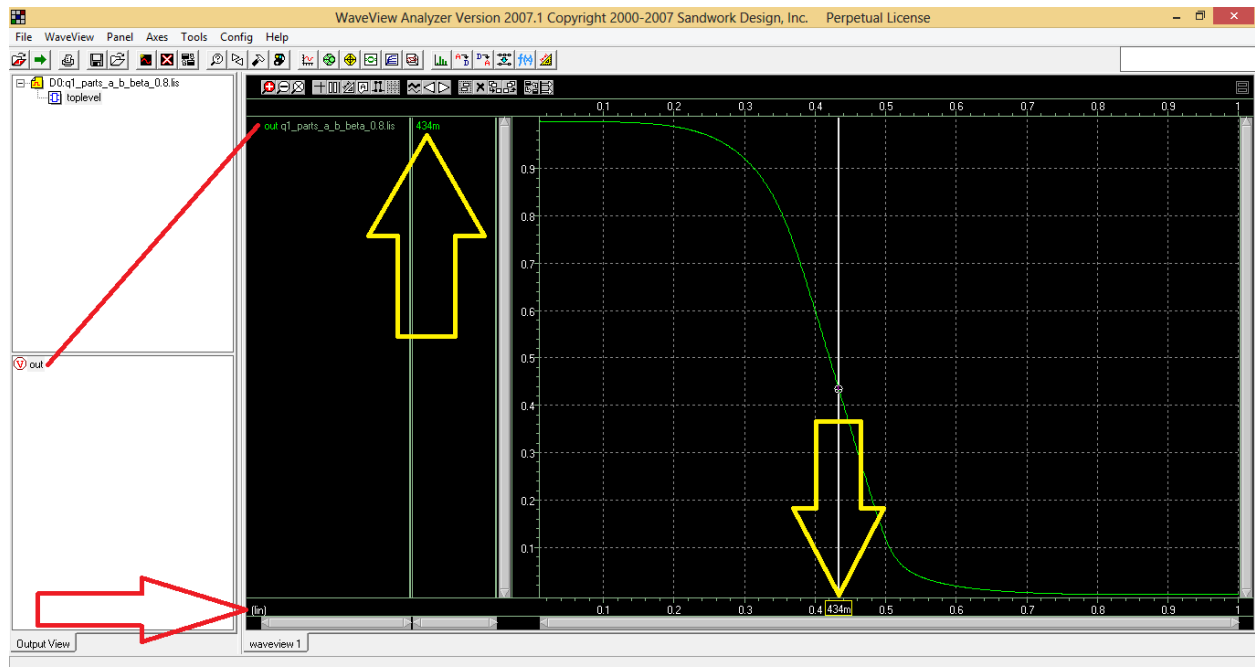

$\Rightarrow V_M = 434 \text{ mv}$

$V_{OH}V_{IL}$ for $\beta = 2$

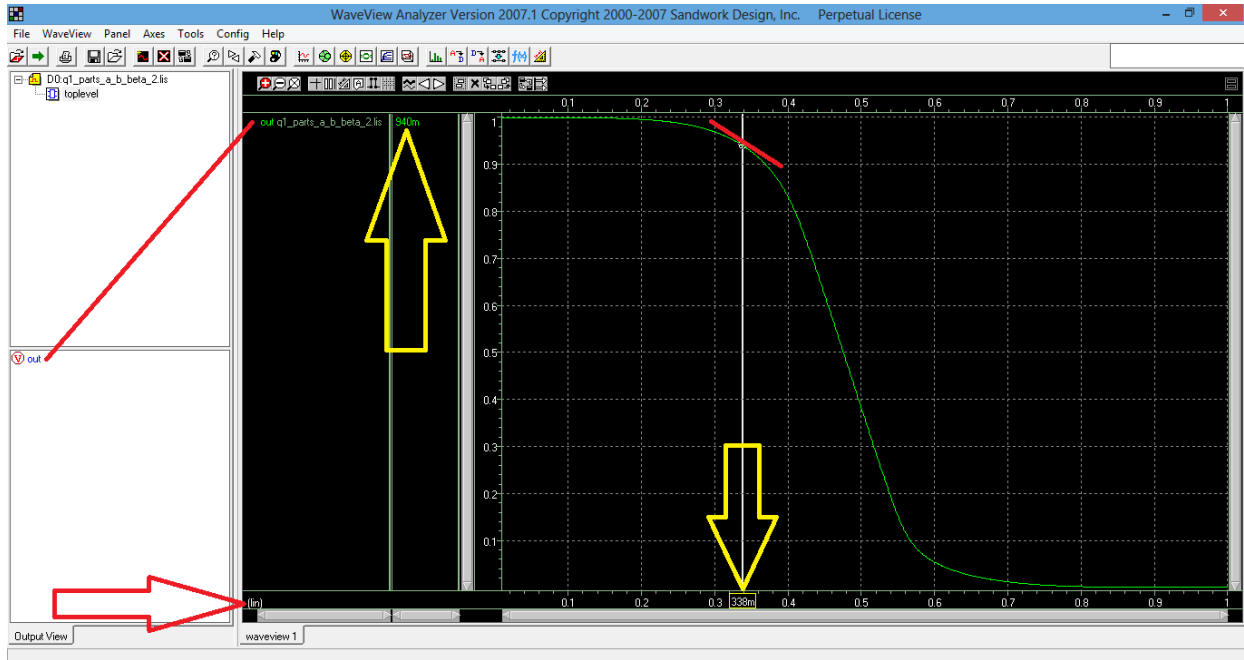


$\Rightarrow V_{OH} = 940 \text{ mv}, \quad V_{IL} = 338 \text{ mv}$

$V_{OL}V_{IH}$ for $\beta = 2$




$\Rightarrow V_{OL} = 67.3 \text{ mV}, \quad V_{IH} = 587 \text{ mV}$

V_M for $\beta = 2$

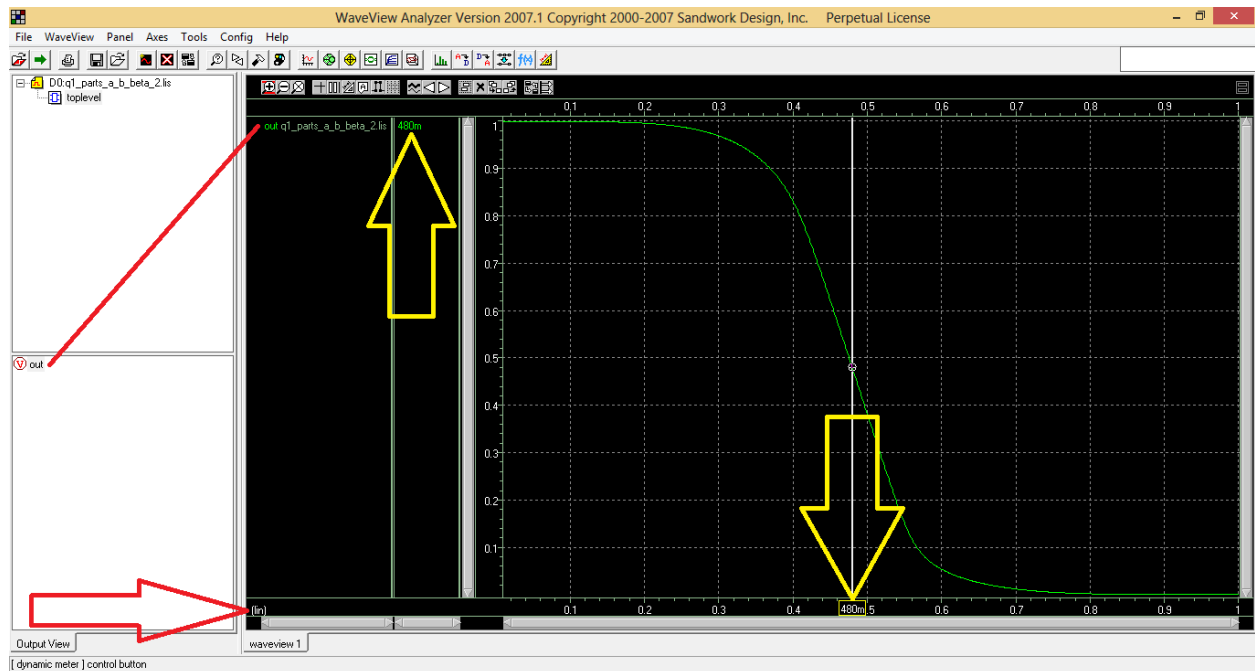


$\Rightarrow V_M = 480 \text{ mv}$

$V_{OH}V_{IL}$ for $\beta = 10$

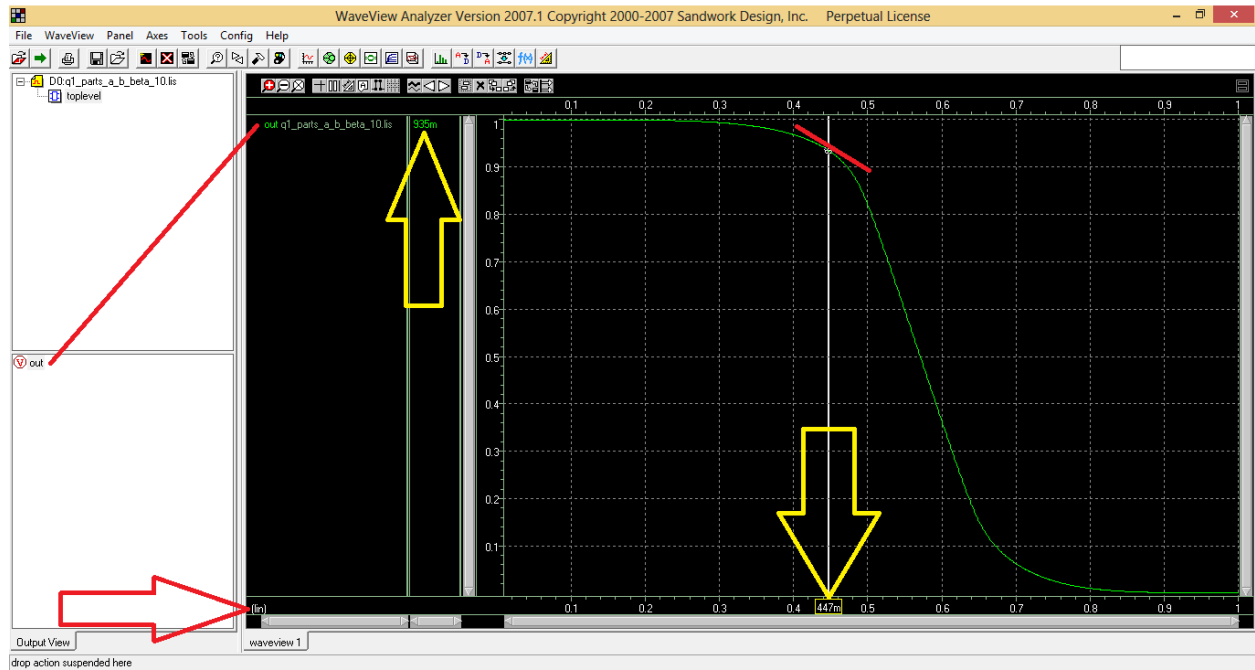


$\Rightarrow V_{OH} = 935 \text{ mV}, \quad V_{IL} = 447 \text{ mV}$

$V_{OL}V_{IH}$ for $\beta = 10$

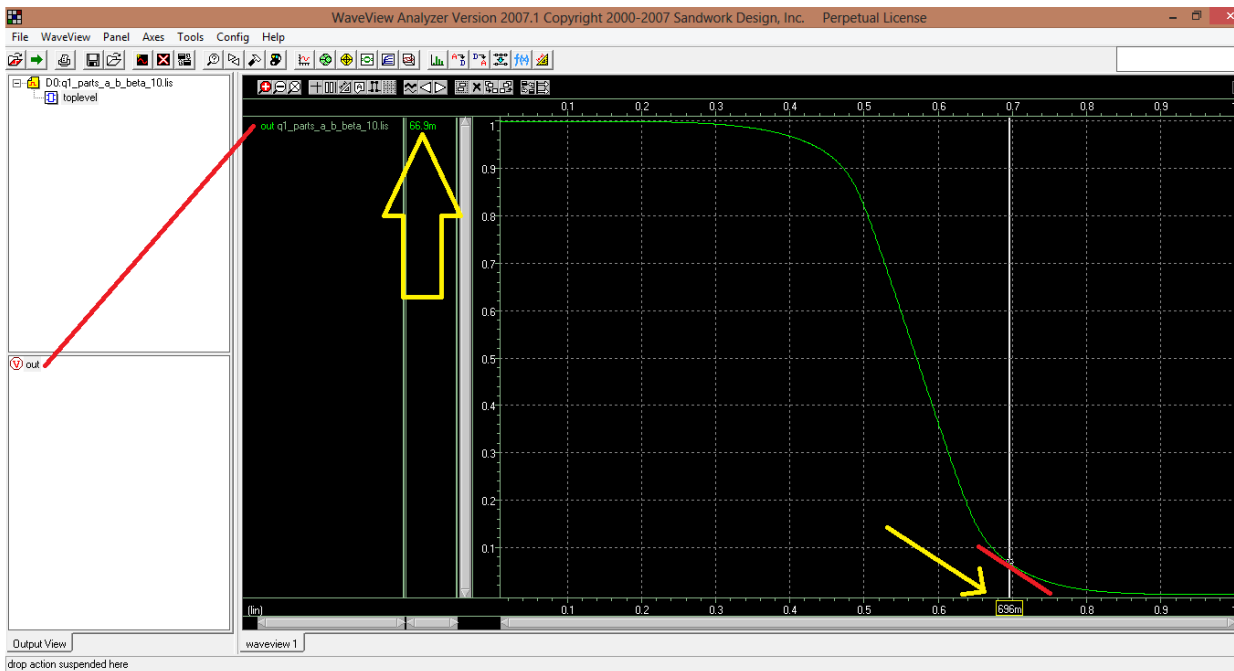

$\Rightarrow V_{OL} = 66.9 \text{ mV}, \quad V_{IH} = 696 \text{ mV}$

V_M for $\beta = 10$

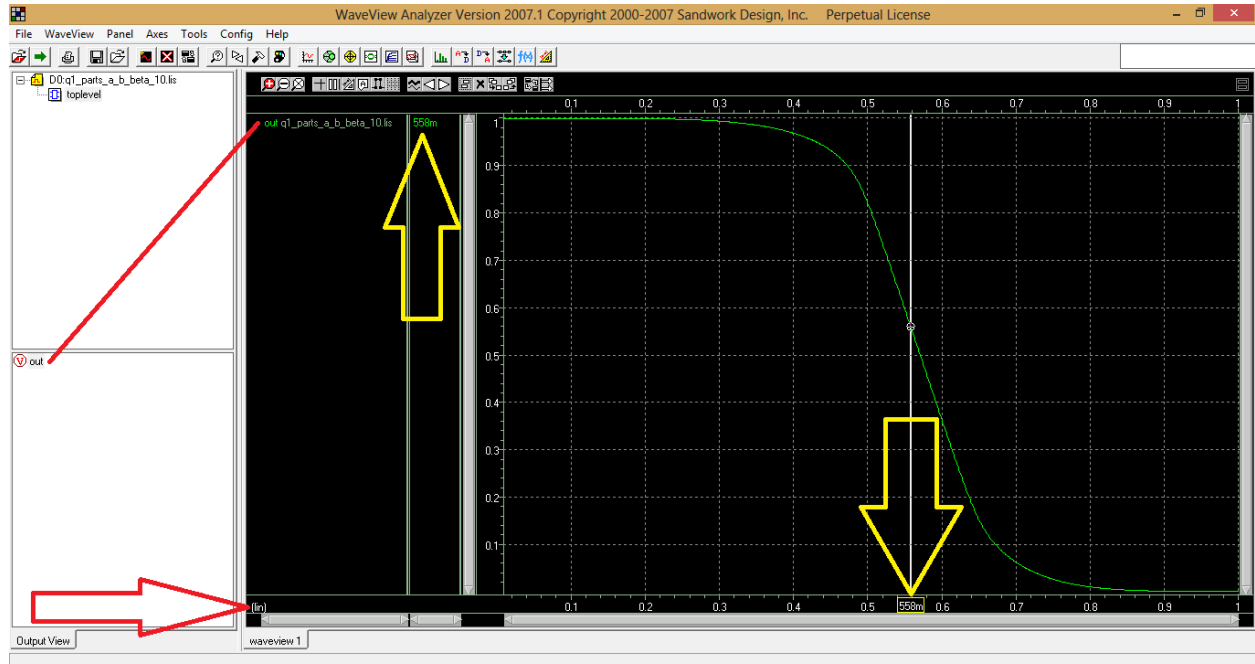


$\Rightarrow V_M = 558\text{ mV}$


β	V_{IL}	V_{IH}	V_{OL}	V_{OH}	V_M
0.8	290 mV	526 mV	59.1 mV	933 mV	434 mV
2	338 mV	587 mV	67.3 mV	940 mV	480 mV
10	447 mV	696 mV	66.9 mV	935 mV	558 mV

Part g:


Output waveform of capacitor(20fF)

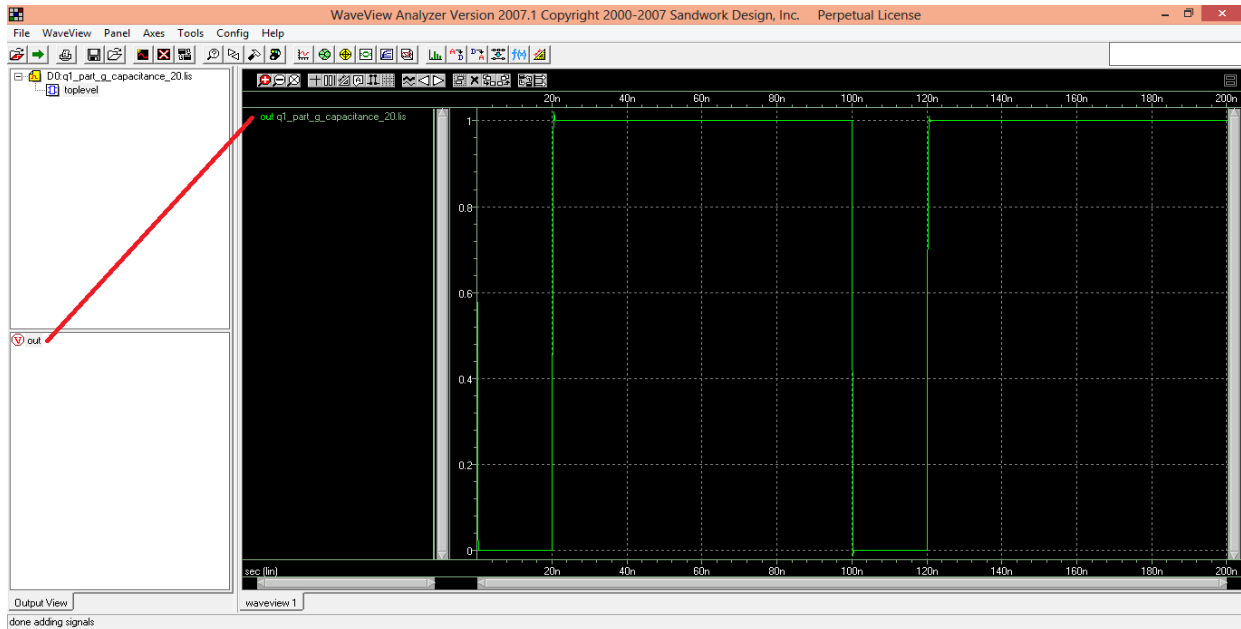

Output waveform of capacitor(50fF)

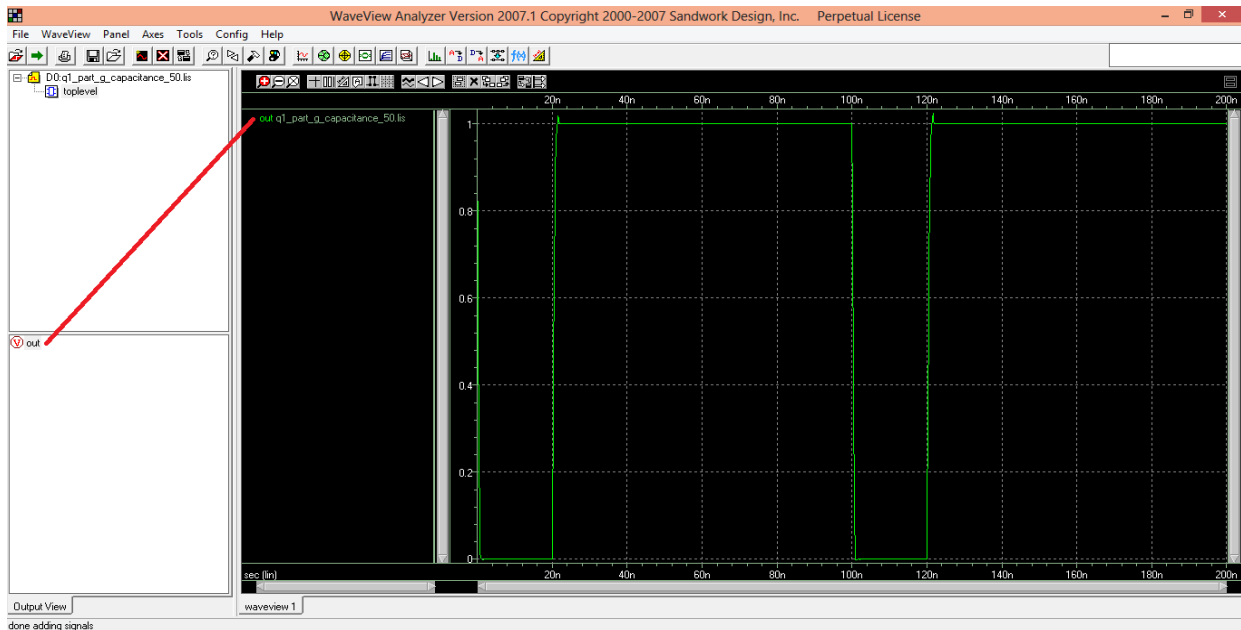

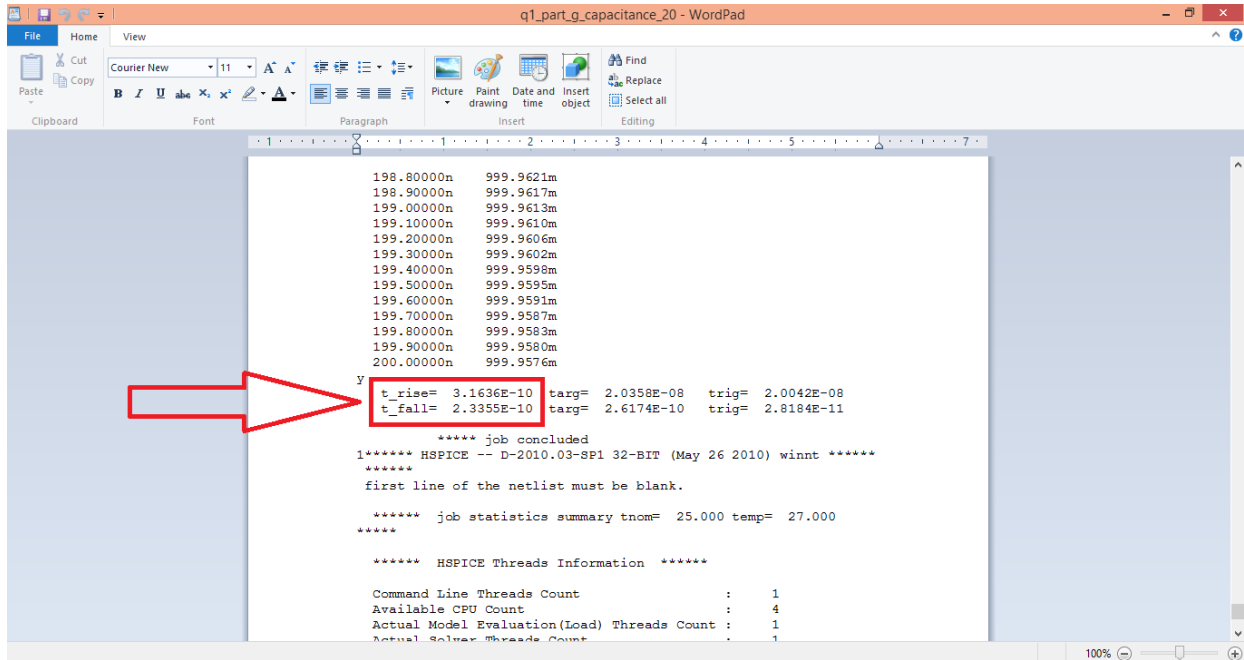T_{rise} , T_{fall} of output voltage of capacitor(20fF)



```
198.80000n 999.9621m
198.90000n 999.9617m
199.00000n 999.9613m
199.10000n 999.9610m
199.20000n 999.9606m
199.30000n 999.9602m
199.40000n 999.9598m
199.50000n 999.9595m
199.60000n 999.9591m
199.70000n 999.9587m
199.80000n 999.9583m
199.90000n 999.9580m
200.00000n 999.9576m
y
t_rise= 3.1636E-10 targ= 2.0358E-08 trig= 2.0042E-08
t_fall= 2.3355E-10 targ= 2.6174E-10 trig= 2.8184E-11
***** job concluded
1***** HSPICE -- D-2010.03-SP1 32-BIT (May 26 2010) winnt *****
*****
first line of the netlist must be blank.


***** job statistics summary tnom= 25.000 temp= 27.000
*****

***** HSPICE Threads Information *****

Command Line Threads Count      : 1
Available CPU Count             : 4
Actual Model Evaluation(Load) Threads Count : 1
Actual Solver Threads Count     : 1
```

$\Rightarrow T_{\text{rise}} = 3.1636\text{E-}10$, $T_{\text{fall}} = 2.3355\text{E-}10$

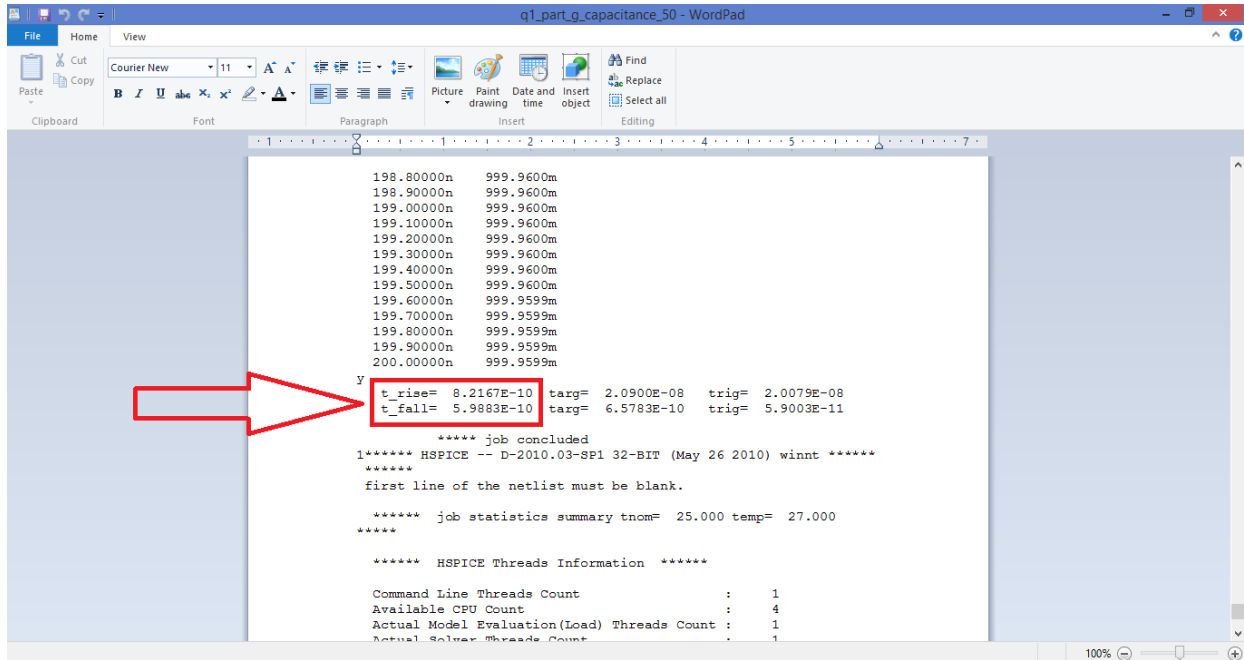T_{rise} , T_{fall} of output voltage of capacitor(50fF)



```

198.80000n 999.9600m
198.90000n 999.9600m
199.00000n 999.9600m
199.10000n 999.9600m
199.20000n 999.9600m
199.30000n 999.9600m
199.40000n 999.9600m
199.50000n 999.9600m
199.60000n 999.9599m
199.70000n 999.9599m
199.80000n 999.9599m
199.90000n 999.9599m
200.00000n 999.9599m
y
t_rise= 8.2167E-10 targ= 2.0900E-08 trig= 2.0079E-08
t_fall= 5.9883E-10 targ= 6.5783E-10 trig= 5.9003E-11
**** job concluded
1***** HSPICE -- D-2010.03-SP1 32-BIT (May 26 2010) winnt *****
*****
first line of the netlist must be blank.

***** job statistics summary tnom= 25.000 temp= 27.000
*****

***** HSPICE Threads Information *****

Command Line Threads Count      : 1
Available CPU Count             : 4
Actual Model Evaluation (Load) Threads Count : 1
Actual Solver Threads Count     : 1
  
```

=> $T_{rise} = 8.2167E-10$, $T_{fall} = 5.9883E-10$

Cap	$t_{fall}(ps)$	$t_{rise}(ps)$
20fF	233.55	316.36
50fF	598.83	821.67


As the capacitance increases, the value of RC(Time Constant) increases, then duration of the transient state($5 \times$ Time Constant) increases, so T_{rise} and T_{fall} increase.

Question 2:


Extracting Model's Parameters from Simulation

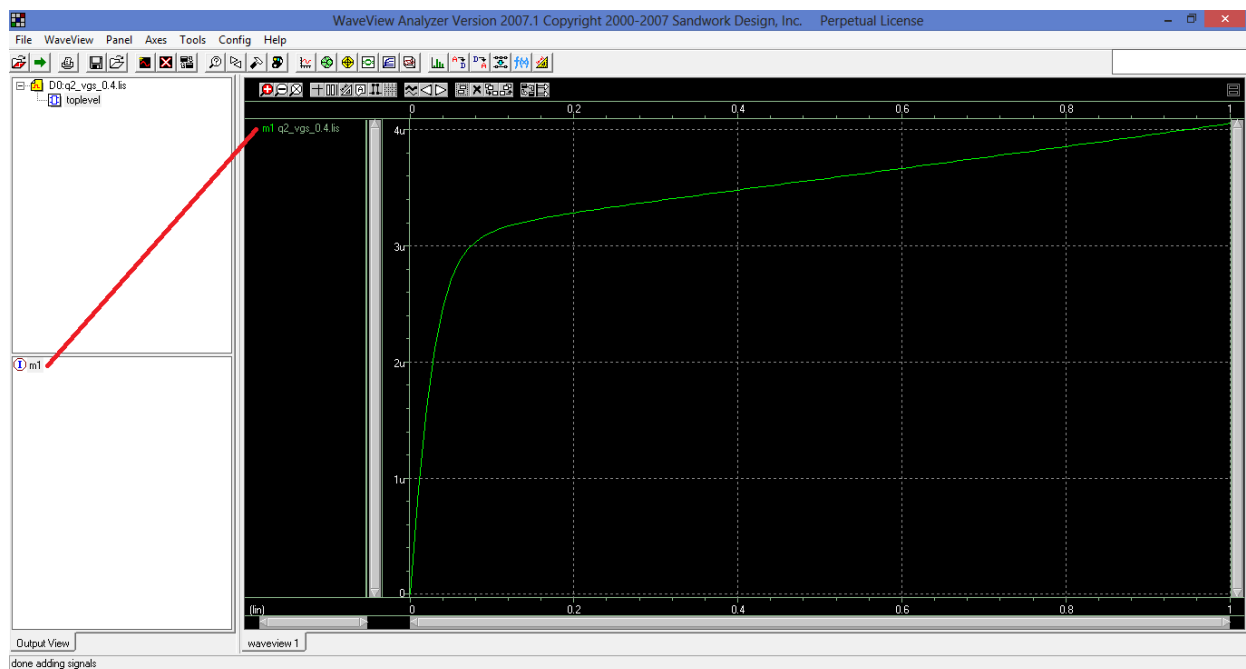Part a:


IV characteristic for $V_{gs} = 0.4\text{v}$



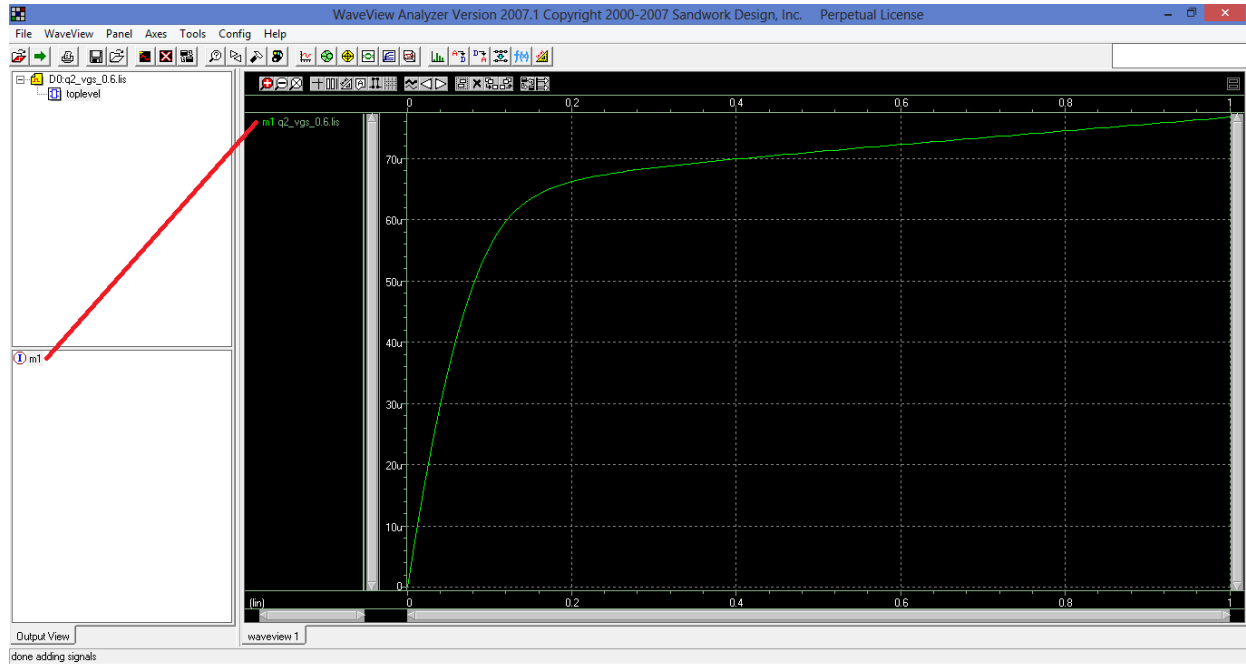
IV characteristic for $V_{gs} = 0.6\text{v}$



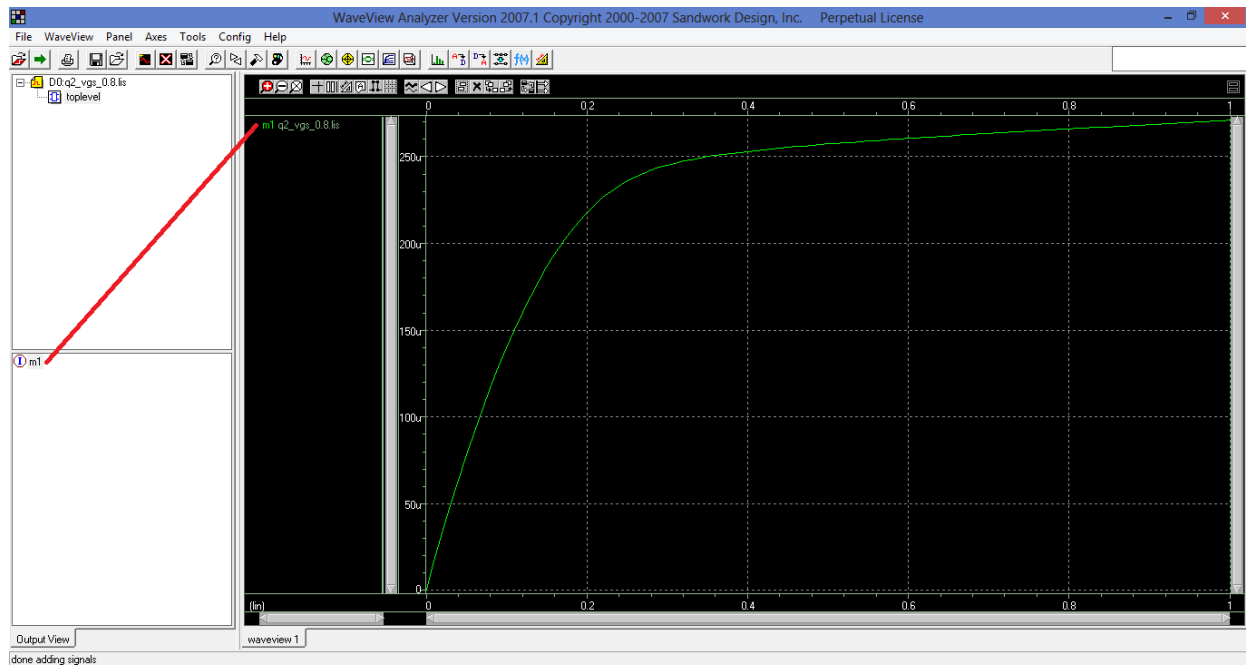IV characteristic for $V_{gs} = 0.8\text{v}$



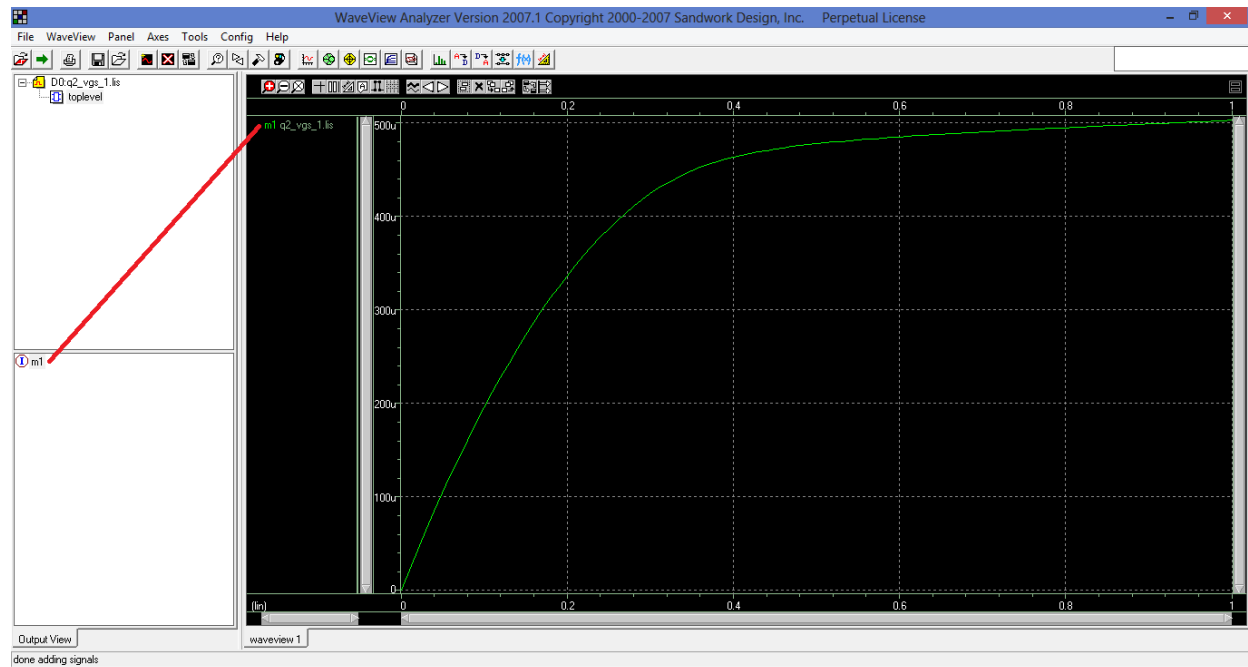IV characteristic for $V_{gs} = 1\text{v}$



Part b:


V_{T0} :

To calculate V_{T0} , we consider 2 points of IV characteristic with the same V_{DS} but different V_{GS} then we have:

$I_{DS1} = I_{DS}$ of first considered point, $I_{DS2} = I_{DS}$ of second considered point

$$\frac{I_{DS1}}{I_{DS2}} = \frac{(V_{GS1} - V_{T0})^2}{(V_{GS2} - V_{T0})^2} \Rightarrow V_{T0} = \frac{\sqrt{\frac{I_{DS1}}{I_{DS2}}} V_{GS2} - V_{GS1}}{\sqrt{\frac{I_{DS1}}{I_{DS2}}} - 1}$$

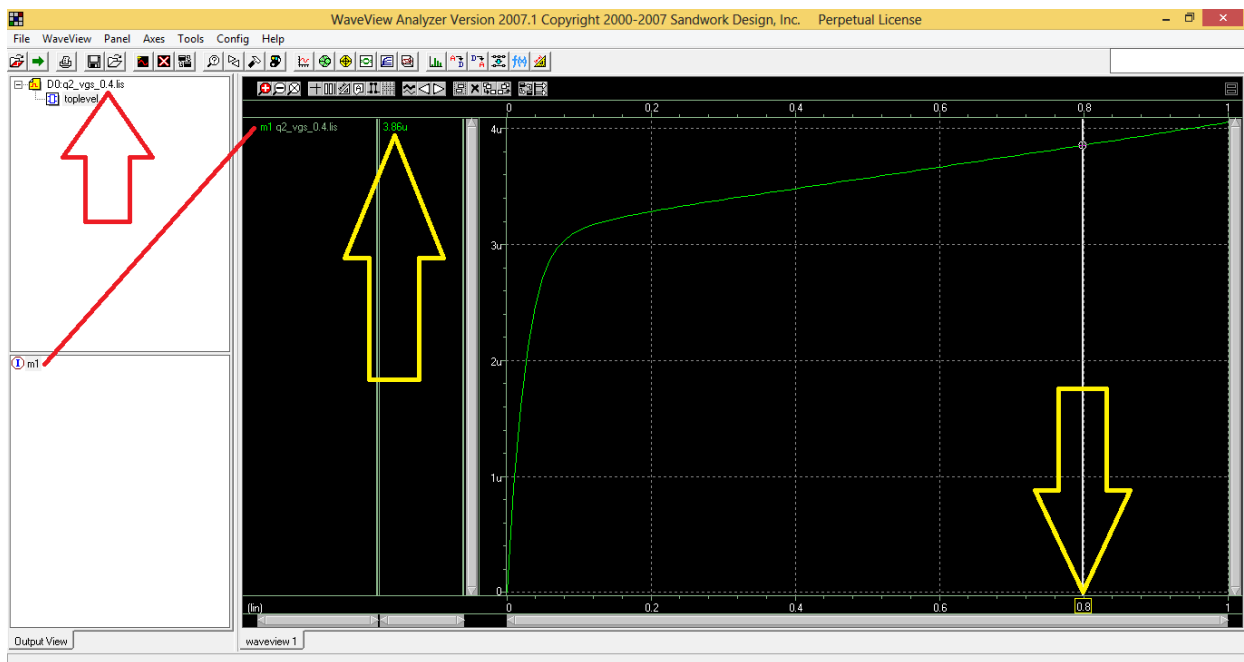First considered point of IV for V_{T0} calculation:



$$\Rightarrow I_{DS1} = 3.86 \text{ uA}, \quad V_{GS1} = 0.8 \text{ v}$$

Second considered point of IV for VT0 calculation:



$$\Rightarrow I_{DS2} = 74.5 \text{ uA}, \quad V_{gs2} = 0.6 \text{ v}$$

$$\Rightarrow VT0 = \frac{\sqrt{\frac{3.86 \text{ uA}}{74.5 \text{ uA}} (0.6 - 0.8)}}{\sqrt{\frac{3.86 \text{ uA}}{74.5 \text{ uA}} - 1}} = 0.34 \text{ v}$$


λ :

To calculate λ , we consider 2 points of IV characteristic with the same V_{GS} but different V_{DS} then we have:

$I_{DS1} = I_{DS}$ of first considered point, $I_{DS2} = I_{DS}$ of second considered point


$$\frac{I_{DS1}}{I_{DS2}} = \frac{1 + \lambda V_{DS1}}{1 + \lambda V_{DS2}} \Rightarrow \lambda = \frac{1 - \frac{I_{DS1}}{I_{DS2}}}{\frac{I_{DS1}}{I_{DS2}} V_{DS2} - V_{DS1}}$$

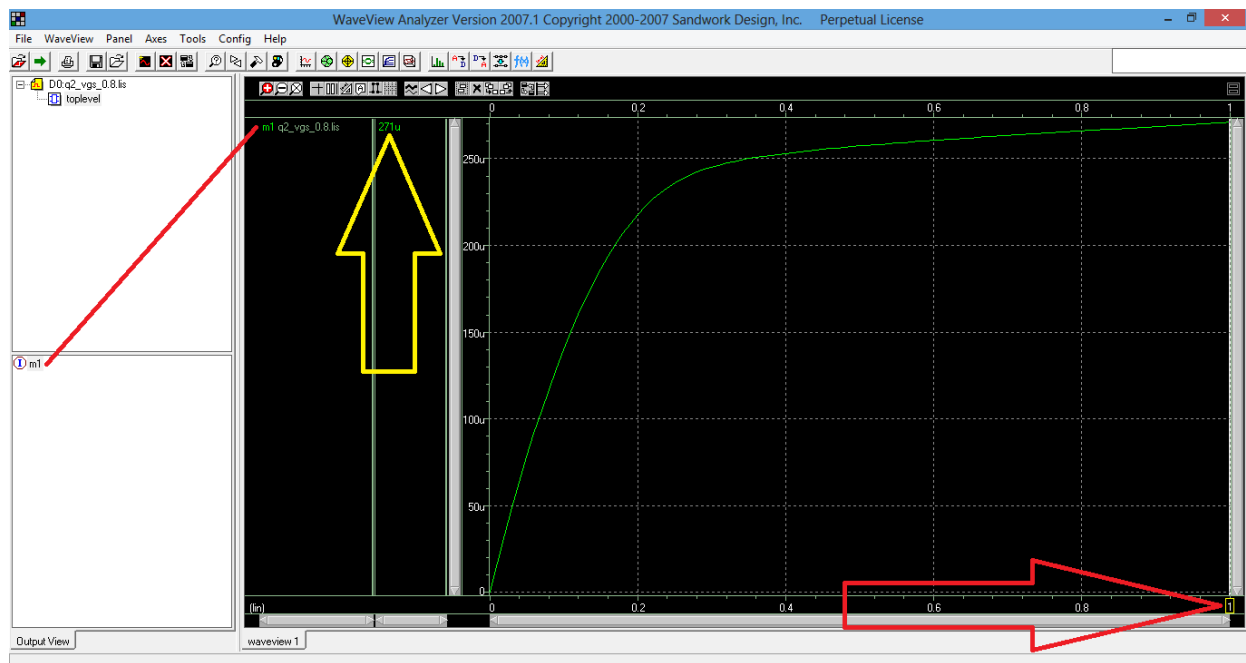First considered point of IV for λ calculation:



$\Rightarrow I_{DS1} = 271 \mu\text{A}, \quad V_{DS1} = 1 \text{ V}$

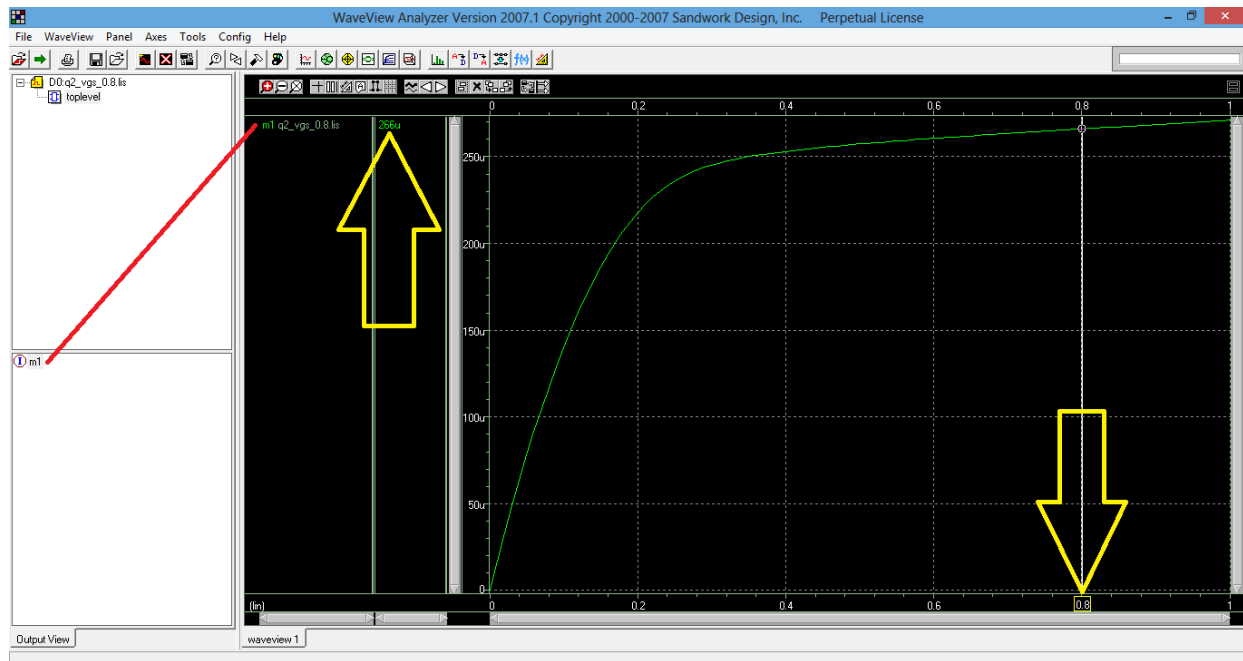Second considered point of IV for λ calculation:



$$\Rightarrow I_{DS2} = 266 \text{ uA}, \quad V_{ds2} = 0.8 \text{ V}$$


$$\Rightarrow \lambda = \frac{1 - \frac{271 \text{ uA}}{266 \text{ uA}}}{\frac{271 \text{ uA}}{266 \text{ uA}} \cdot 0.8 - 1} = 0.1 \text{ V}^{-1}$$

k_p :

To calculate k_p , we consider a single point of IV characteristic in saturation region then we have:

$$k_p = \frac{I_{ds}}{\frac{1}{2} \frac{w}{L} (V_{gs} - V_{T0})^2 (1 + \lambda V_{ds})}$$

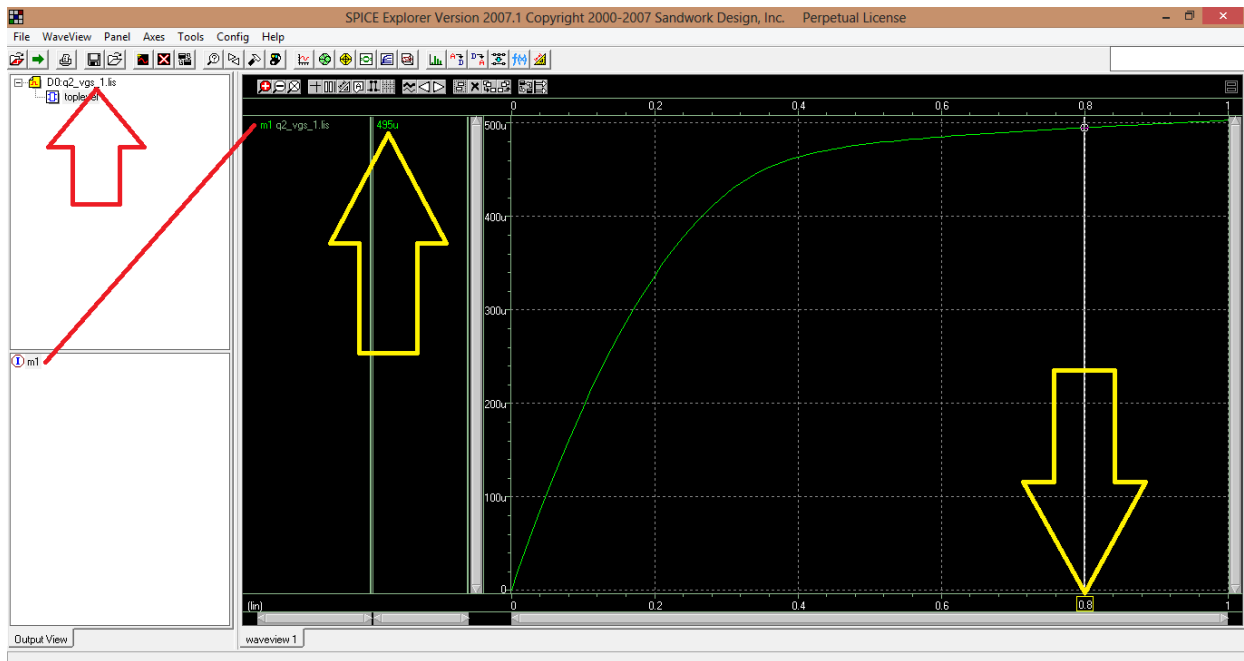single considered point of IV for k_p calculation:




$$\Rightarrow I_{ds} = 495 \mu A, \quad V_{gs} = 1 \text{ V}, \quad V_{ds} = 0.8 \text{ V}$$

$$k_p = \frac{495 \mu A}{\frac{1}{2} \frac{1 \mu}{0.1 \mu} (1 - 0.34)^2 (1 + 0.1 \times 0.8)} = 210 \frac{\mu A}{V^2}$$

V_{T0}	0.34
λ	0.1
k_p	210

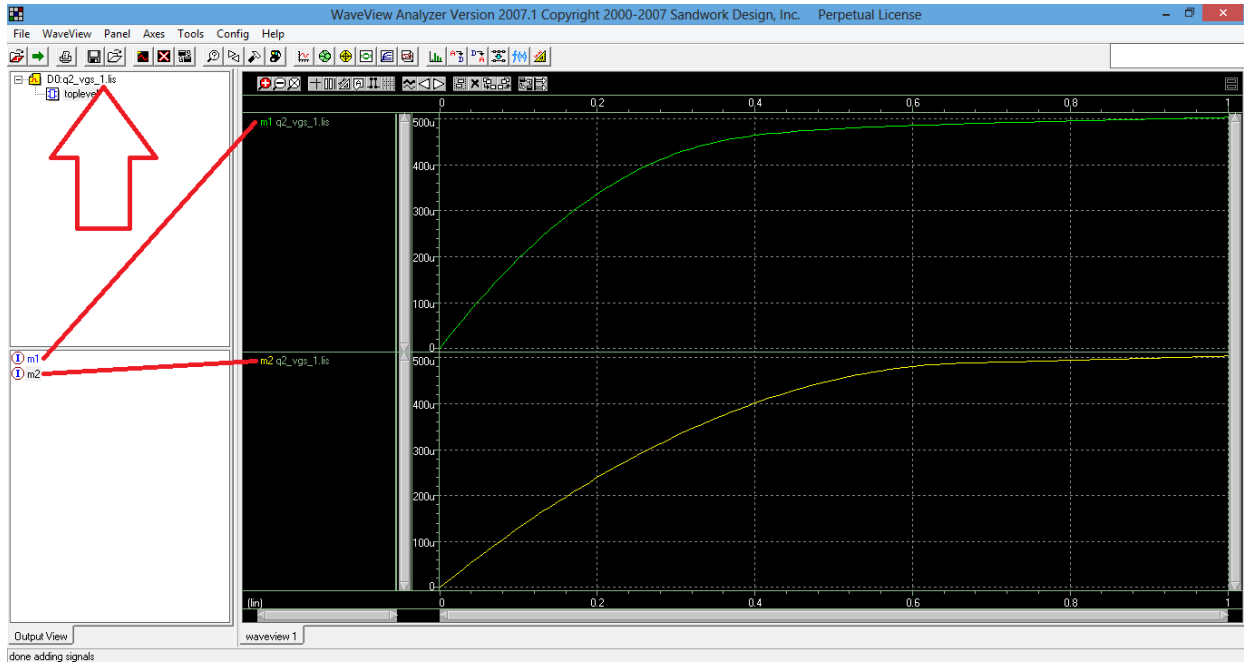
Part g:

IV characteristic of original NMOS and simple NMOS for $V_{gs} = 1\text{v}$




$I_{m1} = I_{DS}$ original NMOS, $I_{m2} = I_{DS}$ simple NMOS

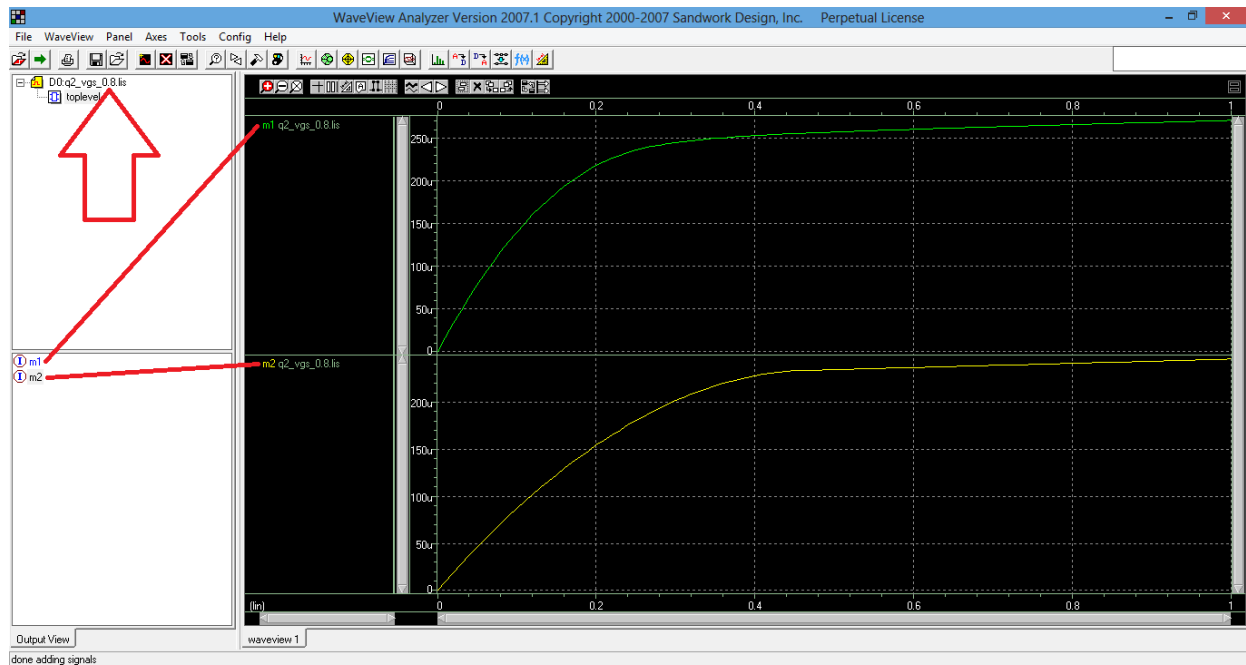
IV characteristic of original NMOS and simple NMOS for $V_{gs} = 0.8v$



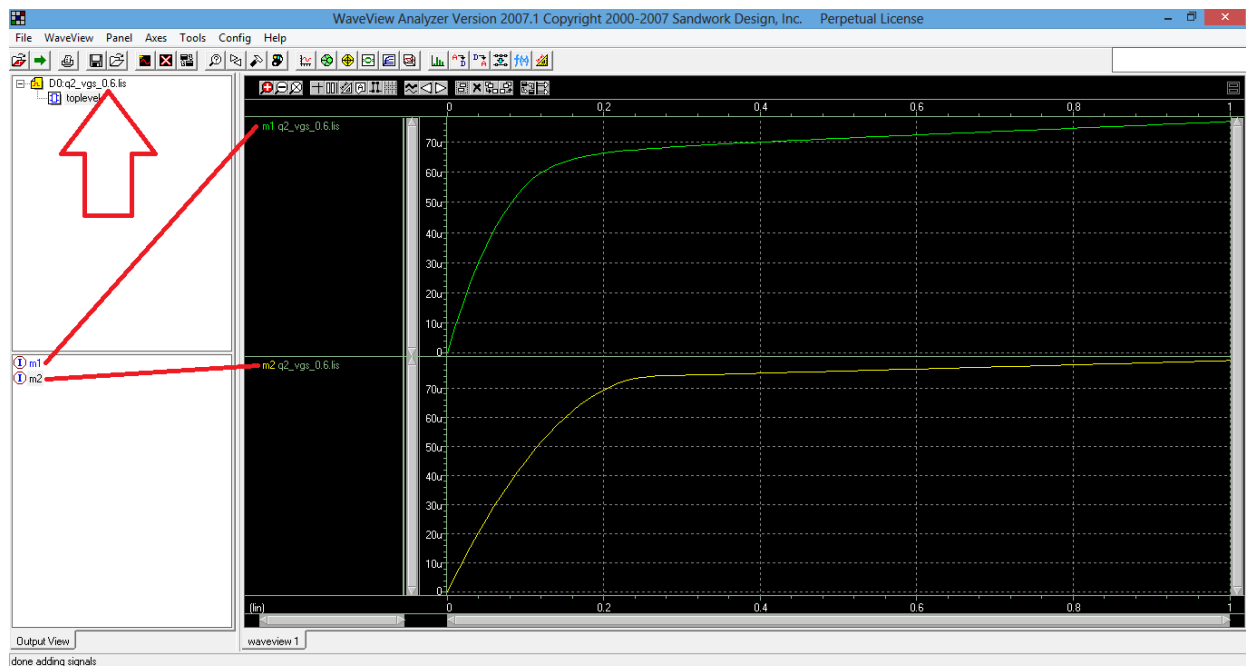IV characteristic of original NMOS and simple NMOS for $V_{gs} = 0.6v$



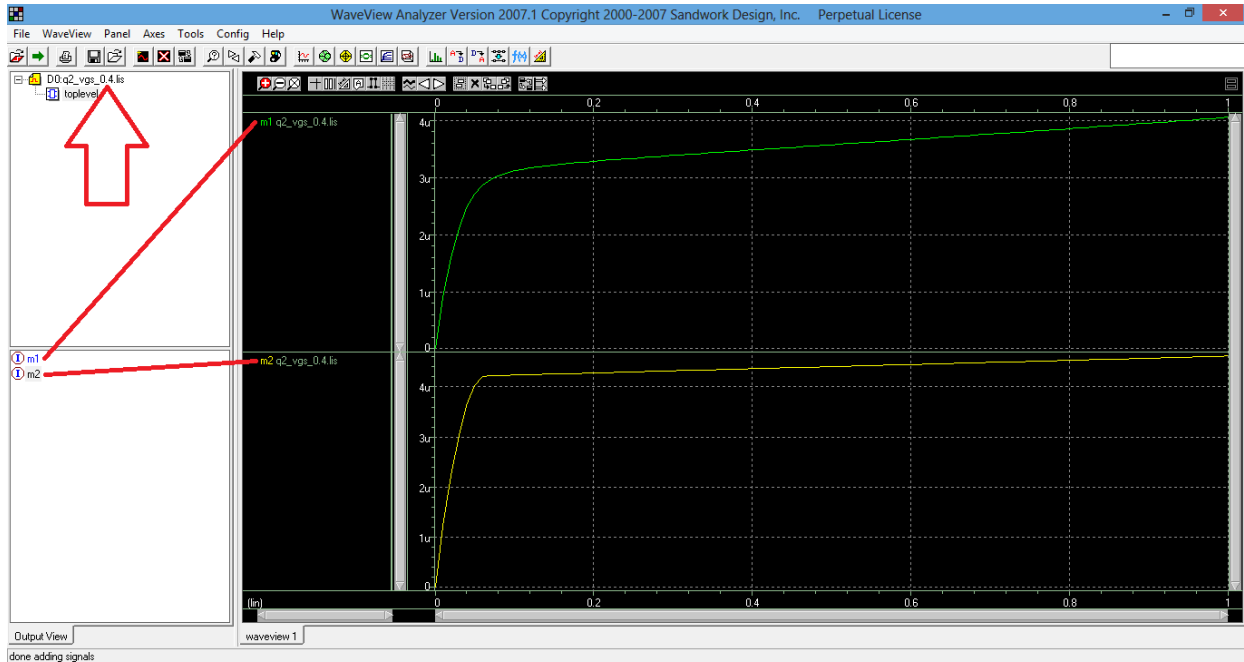IV characteristic of original NMOS and simple NMOS for $V_{gs} = 0.4\text{V}$



As you can see the IV characteristic of original NMOS and simple NMOS are almost same. There is a small difference (about μA) due to the approximation of k_p , λ and V_{T0} and the fact that k_p , λ and V_{T0} are not exactly equal to the original k_p , λ and V_{T0} .